

Diodes


PN junction & MN schottky diodes




FIGURE 2.1 Diode Symbols: (a) PN junction diode, (b) MN Schottky barrier diode

- * Diodes are used in bipolar IC families as actual circuit components
- * Diodes are used as clamping diodes at logic circuits inputs
- * Clamping diodes purpose is to reduce transient voltages that result from switching transitions
- * clamping diodes do not affect normal circuit operation.

 Cross sections for digital IC PN & MN diodes



PN junction diodes

 

MN schottky diode

- * schottky diodes are better than PN junctions diodes in terms of high frequency signal.
- * PN junctions diodes are better than schottky diodes in terms of reverse bias current.

Diode Modelling



Shockley's Current-Voltage Expression

$$I_D = I_S (e^{V_D/\phi_T} - 1) \rightarrow \text{Shockley's equation}$$

$I_S \equiv$ reverse saturation current [A]

$\phi_T \equiv$ thermal voltage [V]

$$\phi_T = \frac{kT}{q}$$

  

$k \equiv$ Boltzmann's constant $= 1.34 \times 10^{-23} \text{ J/K}$

$T \equiv$ temperature [K]

$q \equiv$ elementary electronic charge $= 1.6 \times 10^{-19} \text{ C}$

* The reverse saturation current is the leakage current that flows through a reverse biased diode and is typically $\leq \text{pA}$ for PN junction diodes & $\leq \text{uA}$ for MN Schottky diodes.

Shockley Equation at room temperature.

$$T = 27^\circ\text{C} \text{ or } 300\text{K}$$

$$\phi_T (300\text{K}) = \frac{(1.34 \times 10^{-23})(300)}{(1.6 \times 10^{-19})} = 25.9 \text{ mV}$$

$$e^{V/\phi_T} \approx 40$$

$$I_D(T = 300\text{K}) = I_S (e^{40V_D} - 1)$$

* Note that this equation is valid only at room temperature.

Example 2.1 Relative Forward-Biased PN Junction Diode Current Magnitudes

Use Shockley's expression to determine the diode current for $V_D = 0.1, 0.2, 0.5, 0.7, 0.8, 1,$ and 2.3 V .

Use $I_S = 10^{-14} \text{ A}$ and assume room temperature.

$$I_S = 10^{-14} \quad T = 300\text{K}$$

$$\text{At room temperature } I_D(T = 300\text{K}) = I_S (e^{40V_D} - 1)$$

$$I_D(V_D = 0.1) = (10^{-14})(e^{40(0.1)} - 1) = 536 \text{ fA}$$

$$I_D(V_D = 0.2) = (10^{-14})(e^{40(0.2)} - 1) = 29.8 \text{ pA}$$

$$I_D (V_D = 0.5) = (10^{-14}) (e^{40(0.5)} - 1) = 4.85 \mu A$$

$$I_D (V_D = 0.7) = (10^{-14}) (e^{40(0.7)} - 1) = 14.5 \text{ mA}$$

$$I_D (V_D = 0.8) = (10^{-14}) (e^{40(0.8)} - 1) = 790 \text{ mA}$$

$$I_D (V_D = 1) = (10^{-14}) (e^{40(1)} - 1) = 2.35 \text{ kA}$$

$$I_D (V_D = 2.3) = (10^{-14}) (e^{40(2.3)} - 1) = 9.02 \times 10^{25} \text{ A}$$

Note that for $V_D = 2.3\text{V}$ the diode current is an unprecedented $9.02 \times 10^{25} \text{ A}$ & $I_D V_D$ power dissipated in the diode exceeds the entire power output of our sun!

* Note the diode current's exponential dependence on V_D and:

for $V_D = 0.5 \text{ V} \Rightarrow I_D$ reaches few μAmps

for $V_D = 0.7 \text{ V} \Rightarrow I_D$ reaches mAmps

for $V_D = 0.8 \text{ V} \Rightarrow I_D$ reaches hundreds of mAmps

for $V_D = 1 \text{ V} \Rightarrow I_D$ magnitude is at a normally unobtainable hundreds of amps

for $V_D = 2.3 \text{ V} \Rightarrow I_D$ is unprecedented $9.02 \times 10^{25} \text{ A}$

therefore Power dissipated in the diode $I_D V_D$ exceeds the entire output power of our sun.

Example 2.2 Relative Reverse-Biased PN Junction Diode Current Magnitudes

Use Shockley's expression to determine the diode current for $V_D = -1, -10, -100$, and -200 mV . As in Example 2.1 use $I_S = 10^{-14} \text{ A}$ and assume room temperature.

$$I_S = 10^{-14} \text{ A}, T = 300^\circ \text{K}$$

$$I_D (T = 300^\circ \text{K}) = I_S (e^{40V_D} - 1)$$

$$I_D (V_D = -1 \text{ mV}) = (10^{-14}) (e^{(40)(-1 \text{ m})} - 1) = -392 \times 10^{-18} = -392 \text{ aA}$$

$$I_D (V_D = -10 \text{ mV}) = (10^{-14}) (e^{(40)(-10 \text{ m})} - 1) = -3.3 \text{ fA}$$

$$I_D (V_D = -100 \text{ mV}) = (10^{-14}) (e^{(40)(-100 \text{ m})} - 1) = -9.82 \text{ fA}$$

$$I_D (V_D = -200 \text{ mV}) = (10^{-14}) (e^{(40)(-200 \text{ m})} - 1) = -10 \text{ fA} = -10^{-14} \text{ A}$$

As seen at $V_D \leq -0.2 \text{ V}$ the reverse diode current has a magnitude equal to I_S .

$I_S \equiv$ reverse saturation current.

Note:

$$\left. \begin{array}{l} \therefore \mathcal{E} \gg 1 \quad \therefore I_D(V_D > 0.1) \approx I_S e^{V_D/4r} \\ \therefore \mathcal{E} \ll 1 \quad \therefore I_D(V_D < -0.1) \approx -I_S \end{array} \right\} \text{ (suggested by the two previous examples)}$$

Piecewise Linear Diode Model

* The model has two linear regions

$$I_D = 0 \text{ for } V_D \leq V_D(\text{ON})$$

&

$$V_D = V_D(\text{ON}) \text{ for } I_D \geq 0$$

 


FIGURE 2.3 Piecewise Linear Diode Model: (a) Diode current versus diode voltage, (b) Diode symbol

* for $V_D < V_D(\text{ON})$ the diode is cutoff

* for diodes conducting forward currents $V_D = V_D(\text{ON})$

* for MN schottky diode $V_{SD}(\text{ON}) = 0.3 \text{ V}$ (for silicon)

* Diodes have two modes of operation cutoff & conducting depending on the magnitude & polarity of the diode junction bias V_D .

TABLE 2.1 Diode Modes of Operation

PN Junction Bias	Mode of Operation
Reverse	Cutoff
Forward	Conducting

* The diode breakdown region of operation is avoided in digital circuits & no modeling in this mode is necessary.

Diode capacitance

* A PN junction diode has a capacitance due to charge in depletion region and for forward bias charge stored in the semiconductor bulk regions due to injected minority carriers.

* The capacitance must be fully charged to switch the diode into the conducting state and discharge to switch the diode to the cutoff state.

$$C_D(V_D) = \underbrace{\tau_T \frac{I_S}{\phi_T} e^{V_D/\phi_T}}_{\text{stored minority charge}} + \underbrace{\frac{C_{D0}}{\left(1 - \frac{V_D}{\phi_0}\right)^m}}_{\text{Depletion region charge.}}$$

$C_{D0} \equiv$ zero-bias (i.e. $V_D = 0$) junction capacitance [F]

$\phi_0 \equiv$ junction potential (typically 0.7 to 0.9V) [zero bias]


$m \equiv$ grading coefficient ($m \approx 1/2$ or $1/3$ for digital IC diodes)

$\tau_T \equiv$ minority carrier transit time

* The magnitudes of these parameters can be calculated from the diode's physical attributes and fabrication processing parameters such as doping densities.

Varactor Diodes

* Forward diode voltage $V_D = -V_E$

 


SPICE diode model

SPICE (Simulation Program with Integrated Circuit Emphasis)^{[1][2]} is a general-purpose, open source analog electronic circuit simulator. It is a program used in integrated circuit and board-level design to check the integrity of circuit designs and to predict circuit behavior.

<https://en.wikipedia.org/wiki/SPICE>

 * The large signal diode model used in SPICE shown below



SPICE Diode Model

SPICE Diode DC Characteristic

The nonlinear current source I_D has a value according to the empirically modified Shockley expression

$$I_D' = IS(e^{V_D/N\phi_T} - 1)$$

$N \equiv$ emission coefficient

SPICE Diode Transient Response.

* The transient response of the diode in SPICE is calculated considering the capacitor C_D .

$$C_D = TT \frac{IS}{N\phi_T} e^{V_D/N\phi_T} + \frac{CJO}{\left(1 - \frac{V_D}{VJ}\right)^M}$$

* C_D is equivalently represented as a charge storage element

$$Q_D = TT \times IS(e^{V_D/N\phi_T} - 1) + CJO \int_0^{V_D} \left(1 - \frac{V}{VJ}\right)^{-M} dV$$

* For $V_D > FC\phi_0$

$$C_D = TT \frac{IS}{N\phi_T} e^{V_D/N\phi_T} + \frac{CJO}{\left(1 - \frac{V_D}{VJ}\right)^M} \times \frac{\left[1 - FC(1 + M) + \frac{MV}{\phi_T}\right]}{(1 - FC)^{(1+M)}}$$

TABLE 2.2 SPICE DC Diode Model Parameters

Symbol	Name	Parameter	Units	Default	Typical
I_S	IS	Saturation current	A	1E-14	1E-14
R_S	RS	Parasitic resistance	Ω	0	10
	N	Emission coefficient		1	1

TABLE 2.3 SPICE Transient Diode Model Parameters

Symbol	Name	Parameter	Units	Default	Typical
τ_T	TT	Transit Time	s	0	0.1NS
C_{D0}	CJO	Zero-bias junction capacitance	F	0	2PF
ϕ_0	VJ	Junction potential	V	1	0.8
m	M	Junction grading coefficient		0.5	0.5
	FC	Forward bias depletion capacitance coefficient		0.5	

* For SPICE to calculate transient response one or both of TT & CJO must be specified by the user.

Diode-Resistor Logic (DRL)

* The two logic functions available with diode-resistor logic are AND gates and OR gates.

Diode AND gate.

① D_I - off

② D_I - on

③ D_A - off, D_B - ON or vice versa

State ①

$$V_{out} = V_{DC}$$

What is the V_{IN} value required for D_I to be off.

$$V_{IN} > V_{DC} - V_{D(ON)}$$

State ②




$$V_{out} = V_{D(ON)} + V_{IN}$$

What is the V_{IN} value required for D_I to be ON.

$$V_{IN} \leq V_{DC} - V_{D(ON)}$$

State ③

$$V_{out} = V_{IN} + V_{D(ON)}$$

   

By looking to the possible states of $V_{IN,A}$, $V_{IN,B}$ & V_{out} we can ensure that this DRL gate is an AND gate

$V_{IN,A}$	$V_{IN,B}$	V_{out}
high	high	high
high	low	low
low	high	low
low	low	low


By looking to the table we can see that this gate is AND Gate.

Diode OR gate

① D_I - off

② D_I - ON

③ D_A - ON, D_B - off or vice versa

 


State ①

$$V_{out} = 0V$$

What is the V_{in} value required for D_I to be off.

$$V_{in} < V_D(ON)$$


 


State ②

$$V_{out} = V_{in} - V_D(ON)$$


What is the V_{in} value required for D_I to be ON.

$$V_{in} \geq V_D(ON)$$

  

State ③

$$V_{out} = V_{in} - V_D(ON)$$

 

Example 2.3 Diode-Resistor AND Gate

For the two-input diode-resistor AND gate of Figure 2.6, show that if $V_{IN,A}$ is 1 V above $V_{IN,B}$, D_A is cutoff.

$$V_{IN,A} = V_{IN,B} + 1 \quad \text{--- (1)}$$

$$V_{DA} = V_{out} - V_{IN,A} \quad \text{--- (2)}$$

$$V_{DB} = V_{out} - V_{IN,B} \quad \text{--- (3)}$$

We assume that D_A is conducting (ON)

$$\therefore V_{DA} = 0.7V$$

$$V_{out} = V_{IN,A} + V_{D(ON)} = V_{IN,A} + 0.7 \quad \text{--- (4)}$$

by substitute (4) in (3)

$$V_{DB} = (V_{IN,A} + 0.7) - V_{IN,B} \Rightarrow \text{by substitute (1) in this equation}$$

$$V_{DB} = (V_{IN,B} + 1) + 0.7 - V_{IN,B} = 1.7V$$

But It's not possible for V_{DB} to be 1.7V therefore D_A is not conducting

$\therefore D_A$ is cutoff, D_B is ON

$$V_{out} = V_{IN,B} + 0.7 \quad \text{--- (5)}$$

by substitute (5) in (2)

$$V_{DA} = V_{out} - V_{IN,A} = (V_{IN,B} + 0.7) - V_{IN,A} = V_{IN,B} - V_{IN,A} - 0.7 = -1 + 0.7 = -0.3V$$

$$\therefore V_{DA} < V_{D(ON)}$$


$\therefore D_A$ is cutoff

Diode logic: "IN" or "OUT"

$$IN \equiv OR$$

$$AND \equiv OUT$$

 * Note that OUT & AND have three letters while IN & OR have two letters, This way you can remember that $IN \equiv OR$ & $AND \equiv OUT$.



Level shifted diode-resistor logic.

* voltage degradation. is the offset from the origin with the output and input voltages never zero together.

* voltage degradation is a reduction or increase in the output voltage level by one diode drop $[V_D(ON)]$.

* level shifting diode is a diode included at the output of DRL for voltage degradation correction.

Level-shifted AND Gate

① $D_I - ON$, $D_L - ON$

② $D_I - ON$, $D_L - off$

③ $D_I - off$, $D_L - ON$

④ $D_I - off$, $D_L - off$

state ①

$$V_x = V_{in} + V_D(ON) \quad \text{--- ①}$$

$$V_{out} = V_x - V_D(ON) \quad \text{--- ②}$$

By substitute ① in ②

$$V_{out} = V_{in} + V_D(ON) - V_D(ON)$$

$$V_{out} = V_{in}$$

state ②

$$V_{out} = -V_{EE} = V_{OL}$$

$$V_{in} \leq -V_{EE}$$



state ③

$$V_{out} = V_{CC} - I R_H - V_D(ON)$$

or

$$V_{out} = I R_L - V_{EE} = V_{OH}$$
  
$$I = \frac{V_{CC} - V_D(ON) + V_{EE}}{R_H + R_L}$$



* Since V_{OH} depends on R_H & R_L therefore choosing R_H & R_L value is a matter of design and it will specify V_{OH} value

State ④

* the required conditions for D_I & D_L both to be off is not possible to achieve therefore there is

Level-Shifted OR Gate

① D_I —ON, D_L —ON ② D_I —off, D_L —ON

③ D_I —ON, D_L —off

state ①

$$V_{out} = V_x + V_{D(ON)}$$

$$V_x = V_{in} - V_{D(ON)}$$

$$V_{out} = V_{in} - V_{D(ON)} + V_{D(ON)} = V_{in}$$

state ②

$$V_{out} = V_{cc} - I R_H$$

$$= -V_{EE} + I R_L + V_{D(ON)} = V_{OL}$$

$$I = \frac{V_{cc} - V_{D(ON)} + V_{EE}}{R_L + R_H}$$

State ③

$$V_{out} = V_{cc}$$

$$V_{out} = V_{OH}$$

Example 2.4 Level-Shifted Diode-Resistor AND Gate

Find the output low and high voltages for the level shifted diode-resistor AND gate shown in Figure 2.8a. Use $V_{CC} = 4\text{ V}$, $-V_{EE} = -4\text{ V}$, $V_{D(ON)} = 0.7\text{ V}$, $R_H = 1\text{ k}\Omega$, and $R_L = 2\text{ k}\Omega$.

$$V_{CC} = 4\text{ V}, \quad V_{EE} = 4\text{ V}, \quad V_{D(ON)} = 0.7\text{ V}$$

$$R_H = 1\text{ k}\Omega, \quad R_L = 2\text{ k}\Omega$$

$$V_{OL} = -V_{EE} = -4\text{ V}$$




$$V_{OH} = I R_L - V_{EE} = V_{CC} - I R_H - V_{D(ON)}$$

$$I = ?$$

$$I = \frac{V_{CC} - V_{D(ON)} + V_{EE}}{R_H + R_L} = \frac{4 - 0.7 + 4}{3\text{ k}} = 2.43\text{ mA}$$


$$V_{OH} = I R_L - V_{EE} = 2.43\text{ m} \times 2\text{ k} - 4 = 0.87\text{ V}$$

no state ④ for this gate circuit

   


Clamping Diodes

 - * When input to a gate is switched high to low the input voltage sometimes swings beyond 0V. this called **ringing** and may cause physical damage to the gate itself.
- * Connecting diodes to each input of a gate reduces these problems by preventing the inputs from falling below one diode drop of -0.7V



Level-Shifting Diodes

 - * it used to level shift the output voltage.
- * another use of diode forward voltage is to ensure that sub-circuits with complementary objectives are not conducting simultaneously.



م. (صالح الشبيبي)